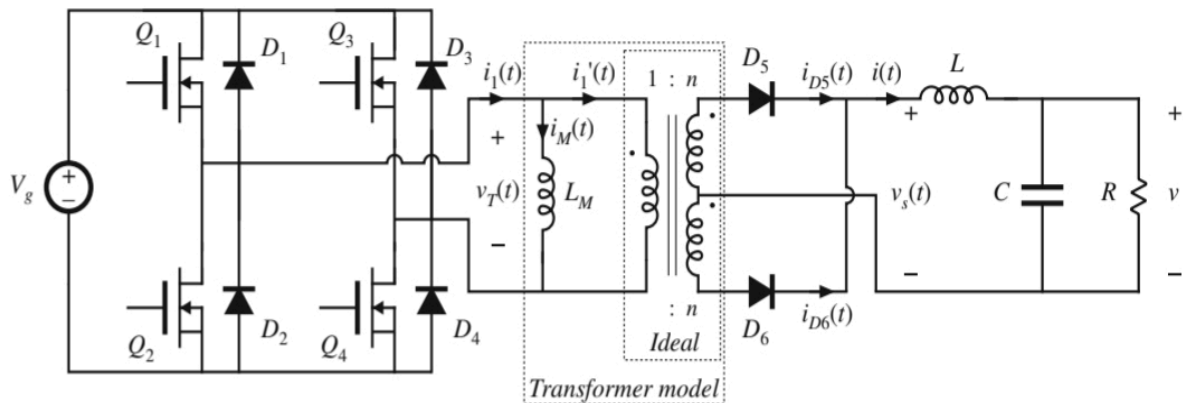


Objective: Close loop control of a 1kW Full bridge Isolated buck converter for EV battery charging with 400V input and 48V output.

Circuit diagram:




Assumptions:

- Transformer ratio $1:n = 1:1/2$
- Switching frequency (f_s) = 20kHz
- Inductor Current ripple = 10% of load current
- Output voltage ripple = 2% of load voltage
- Negligible leakage inductance

System is designed to achieve:

- phase margin $\geq 55^\circ$
- $t_{ss} \leq 5\text{msec}$
- Steady state error for step input $\leq 0.01\%$

Waveform:

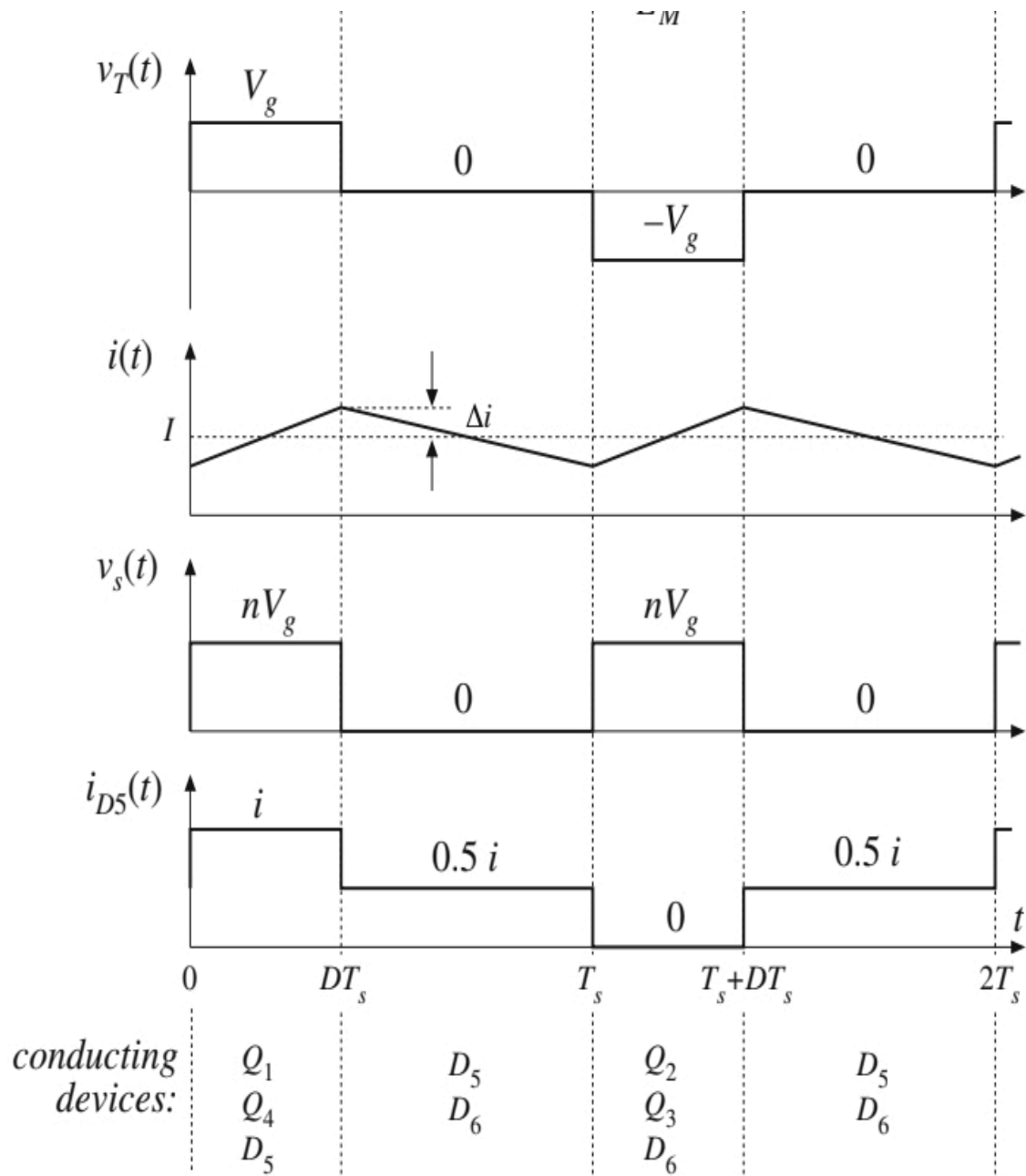

Calculation of Capacitance and inductance:

Data given:

$$V_o = 48V, V_g = 400V, n = 0.5, I_o = 20.83A, \Delta I_L = 2.083A$$

$$\Delta V_o = 0.96V, T_s = 1/f_s$$

$$R = 2.304\Omega$$

$$V_o = n \cdot D \cdot V_g$$

$$D = 0.24$$

$$\bullet \Delta I_L = \frac{(nV_g - V_o) \cdot D \left(\frac{T_s}{2}\right)}{(2L)} = 2.083A$$


$$L = 218.91\mu H$$

$$\bullet \Delta V_o = \frac{\Delta I_L \cdot \frac{T_s}{4}}{2C} = 0.96V$$

$$C = 6.78\mu F$$

Open loop system transfer function:
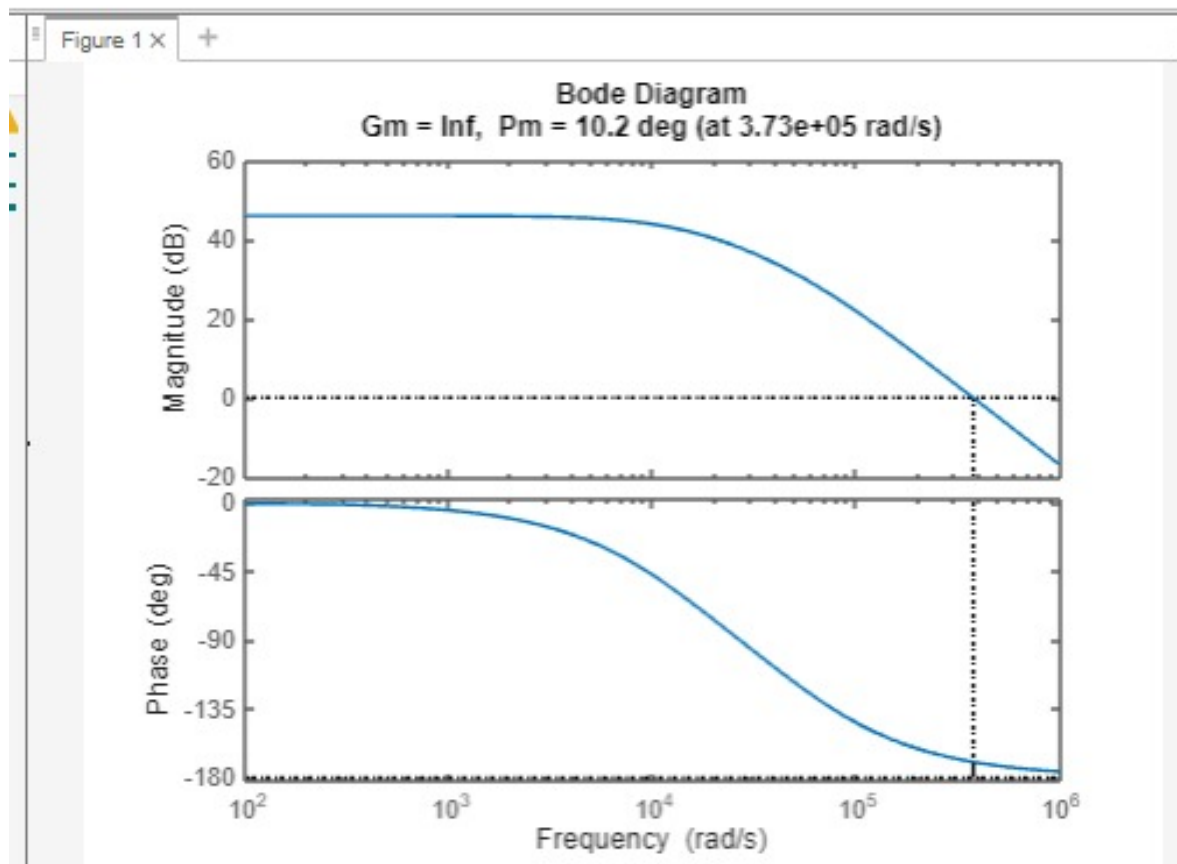
$$\frac{v(s)}{d(s)} = \frac{nVg}{LCs^2 + \frac{L}{R}s + 1}$$



Bode plot of open loop system transfer function using MATLAB

- phase margin is 10.5°
- Since phase margin is not as desired, compensator design is required

Compensator design of Full bridge Isolated Buck converter:

- $\text{error} = \frac{1}{K_{req}} = \frac{0.01}{100}$

$$K_{req} = 10000$$

$$K_{comp} = 50$$

- $t_{ss} = \frac{4msec}{W_c}$, $W_c \geq 800 \text{ rad/sec}$


- Let the W_c be at 800 rad/sec

- $H_c(s) = k_{comp} * \frac{1 + \frac{s}{w_z}}{1 + \frac{s}{w_p}}$


From bode plot analysis:

$$w_p = 0.08 \text{ rad/sec}$$

$$w_z = 8000 \text{ rad/sec}$$

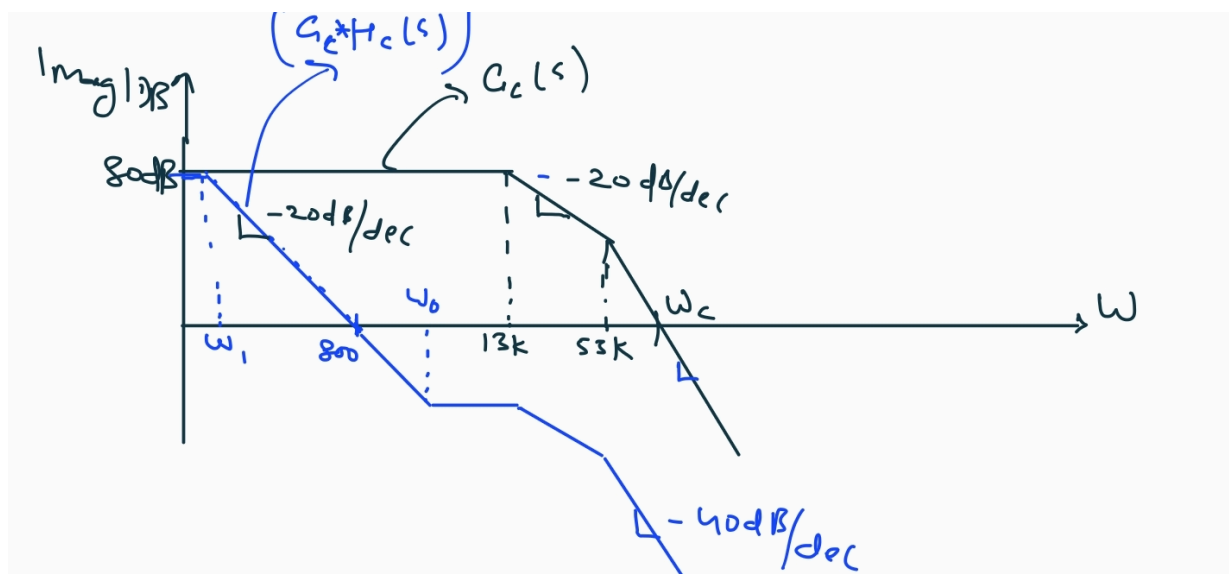


Bode plot of system with compensator:

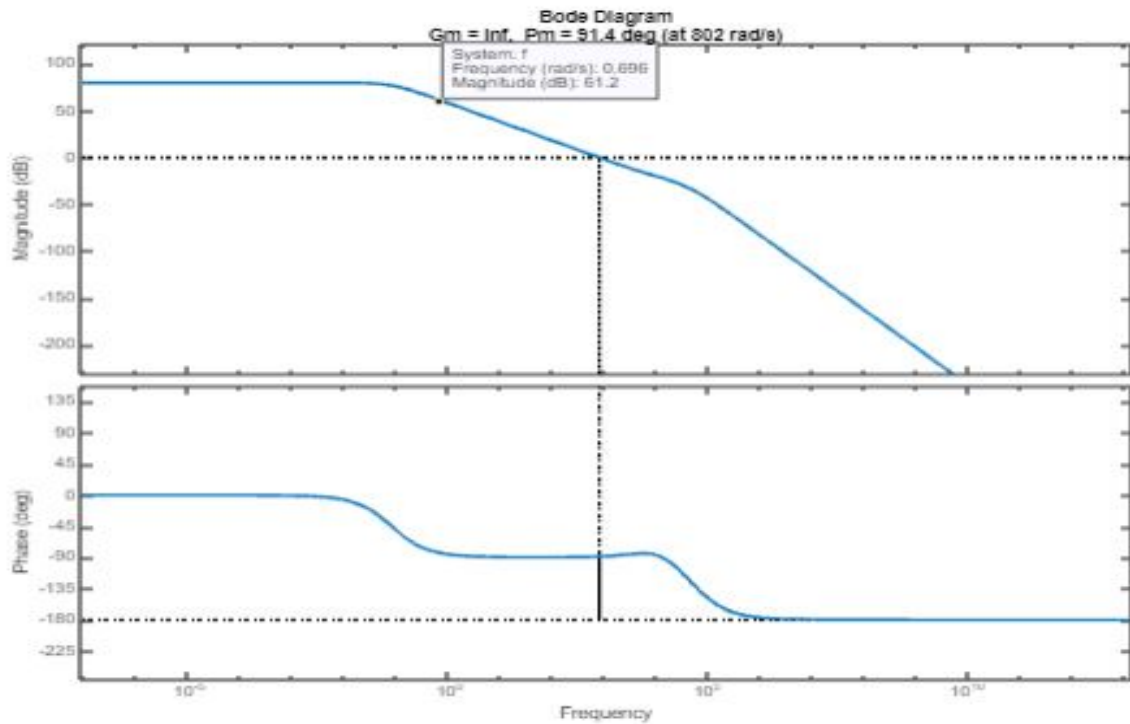

Bode plot using MATLAB


- phase margin is 91.4°
- ω_c is 802 rad/sec, so time to reach steady state is 5 msec.
- Thus the compensator design meets the system specifications.

Schematic for simulation in MATLAB:

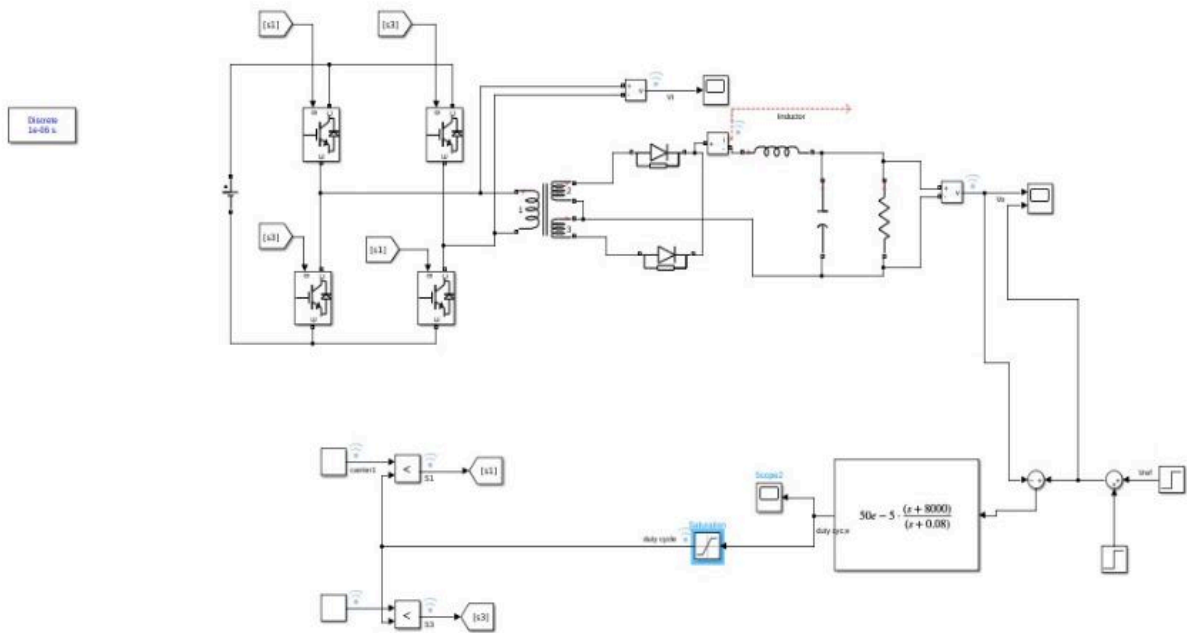


Simulation Results:

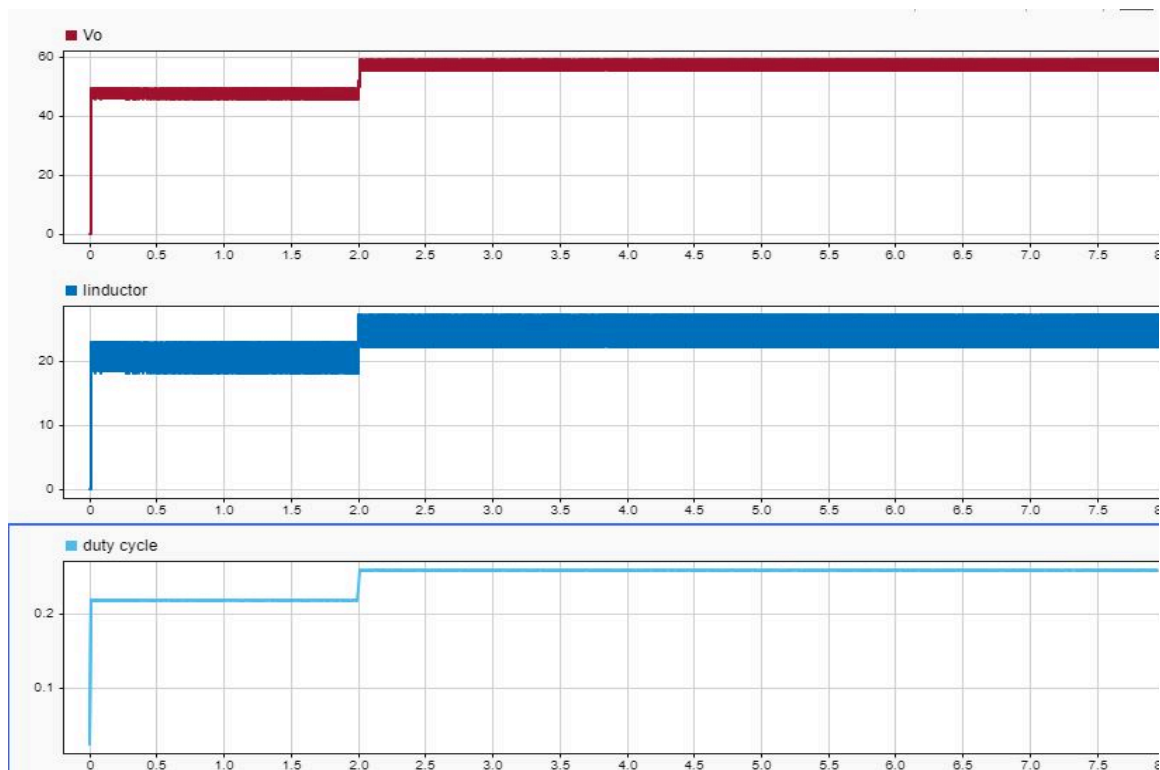
Output voltage, Inductor current, duty cycle



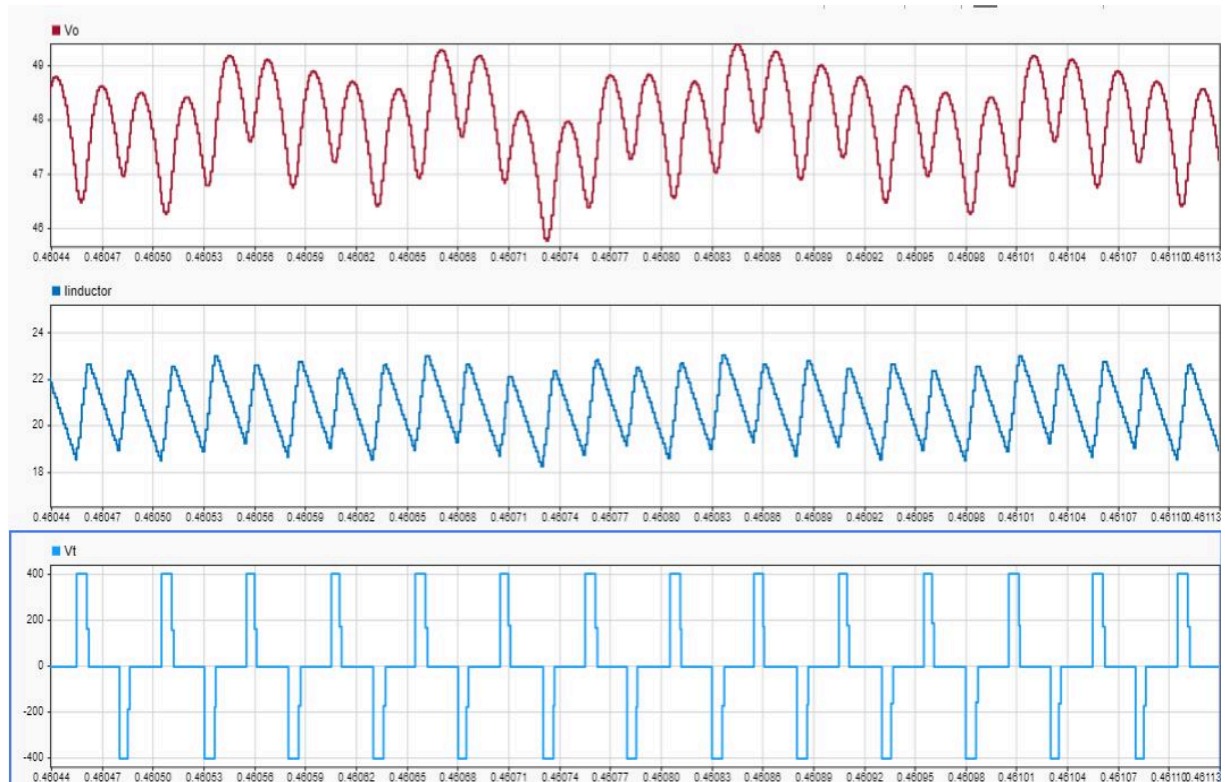Voltage ripple, Current ripple, Transformer primary voltage




Step response:

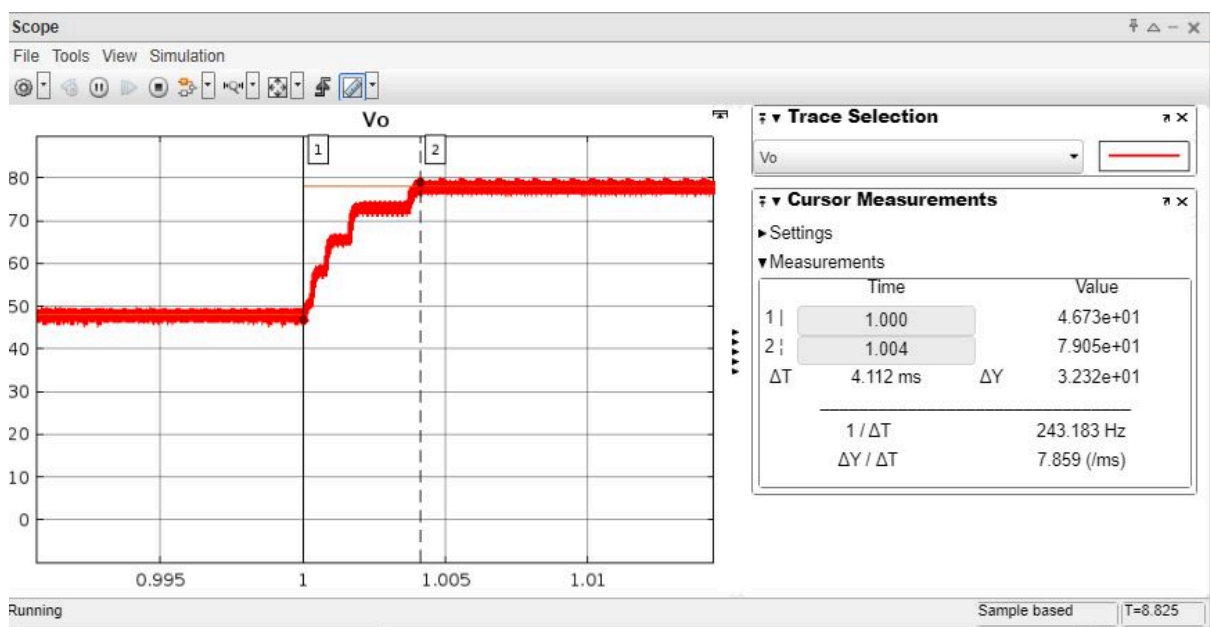

Switch selection:

- Required blocking voltage of all the switches is 400V and conduction current rating is 11.45A .
- Selecting safety factor as 1.5.
- Voltage rating of switches =600V
- Current rating of switches = 18A
- Voltage rating of diode = 300V
- Current rating of diode = 35A

Selected IGBT's mfr part no.: STGD10HF60KD

STGD10HF60KD	
	Mouser No: 511-STGD10HF60KD
	Mfr. No: STGD10HF60KD
	Mfr.: STMicroelectronics
	Customer No: <input type="text" value="Customer No"/>
	Description: IGBT Transistors Automotive-grade 10 A, 600 V short-circuit rugged IGBT Ultrafast diode

Unit price: 243 INR

Selected diode part no.:1N1187GN-ND

1N1187

DigiKey Part Number	1N1187GN-ND
Manufacturer	GeneSiC Semiconductor
Manufacturer Product Number	1N1187
Description	DIODE GEN PURP 300V 35A D05

Unit price: 519 INR

Conclusion:

The system is well designed to meet the requirements.